

Projet ETI :

Dossier Technique :

Le synthétiseur musical

Boust Sylvain
Briosne Fréjaville Clémence
Gr 2

Cahier des charges :

- Pouvoir émettre des sons : 7 notes de la gamme de DO Majeur
- Réaliser une enveloppe en amplitude à l'émission de chacun de ces sons
- Pouvoir jouer une mélodie

Solutions techniques :

- Création des fréquences à l'aide de l'horloge présente sur la carte DEO et d'un compteur : Programmes VHDL *compteur17bitsdo*, *compteur16bitsla*, *compteur17bitsre*...
- Les notes sont jouées grâce aux interrupteurs: création d'un multiplexeur en VHDL *Multiplexer_VHDL*
- Création d'une mélodie : Programme VHDL *mélodie*
- Choisir entre jouer une note avec un interrupteur ou jouer la mélodie : Programme VHDL *choix*
- Programmation des entrées du circuit de modulation en amplitude : Programme VHDL *ampli*

 
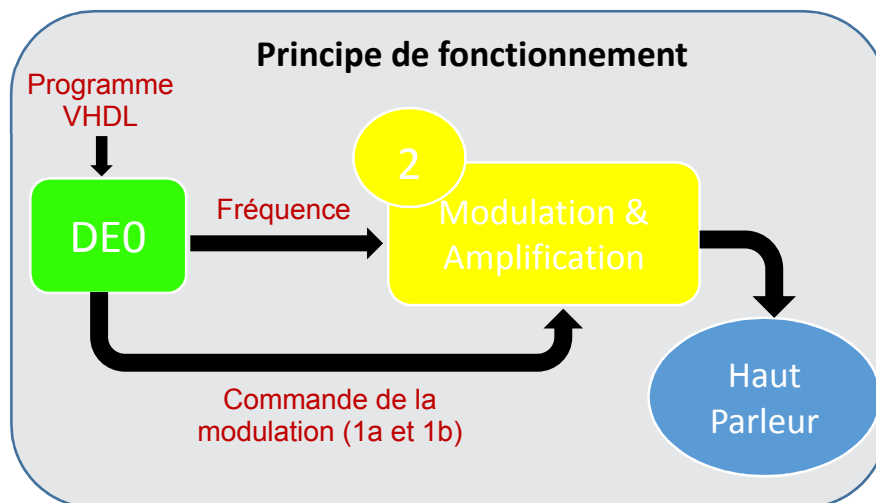


Figure 1 Photo de la maquette

- Circuit de modulation de l'amplitude : DG200a et TL071 (amplificateur opérationnel)

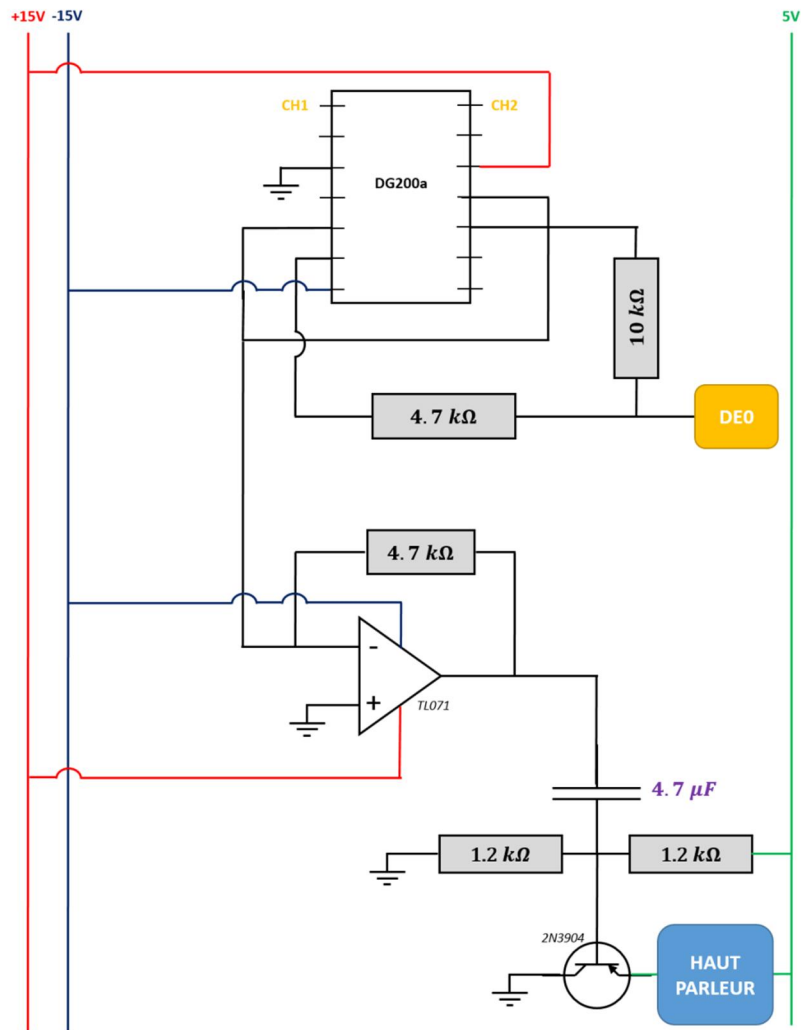


Figure 2 Circuit du synthétiseur

La carte DE0 fournit la fréquence en entrée du circuit qu'on souhaite entendre, le programme VHDL est détaillé à la fin du dossier.

Le composant DG200a est la clé de la modulation, en effet les entrées CH1 et CH2 pilotées par un code VHDL permettent de fournir en sortie différentes tensions de manière précise. Le DG200a est à logique négative, si CH1 et CH2 sont reliées à la masse, alors la tension de sortie est maximale.

Valeur de CH1	Valeur de CH2	Valeur de la sortie par rapport à l'entrée
Masse	Masse	150 %
Masse	Positif	100%
Positif	Masse	50%
Positif	Positif	0%

Pour pouvoir amplifier jusqu'à 150%, ce circuit de modulation nécessite un amplificateur opérationnel, et le TL071 répond parfaitement aux besoins du circuit.

Avant de finir au hautparleur, le signal est une dernière fois amplifié par un transistor.

Observations sur l'oscilloscope :

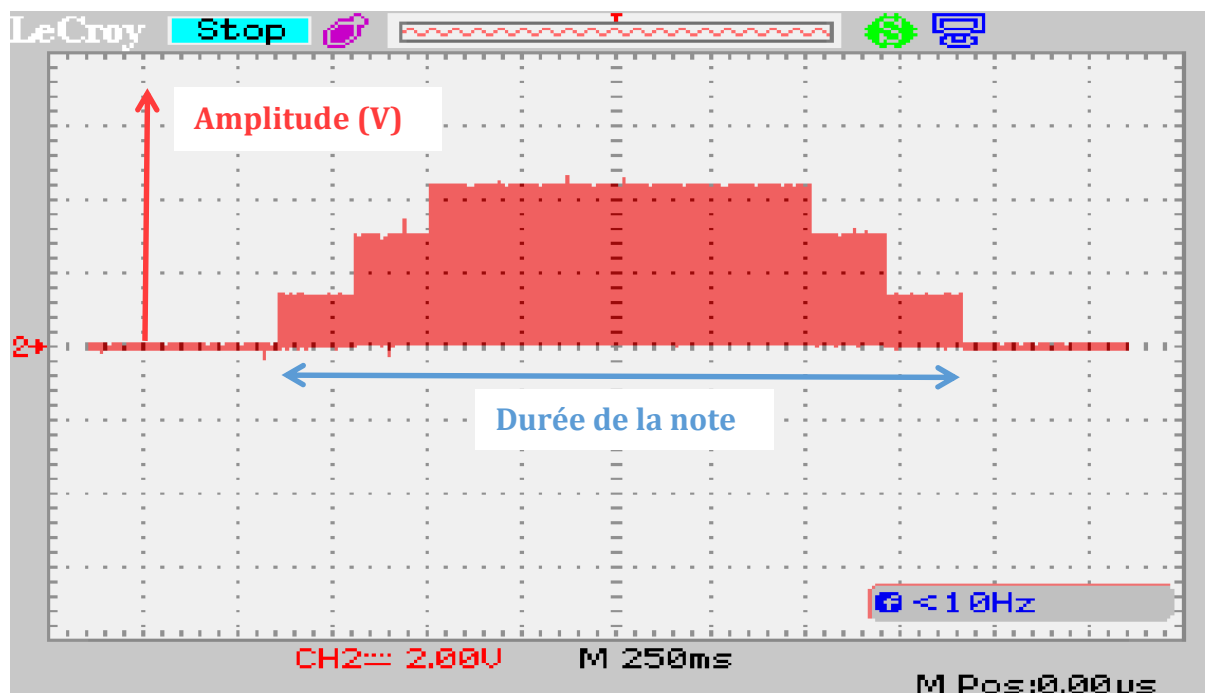


Figure 3 Observation de la variation d'amplitude

On observe bien une variation de l'amplitude du signal qui croit progressivement, puis décroît.

Programmes VHDL

● Diagramme blocks

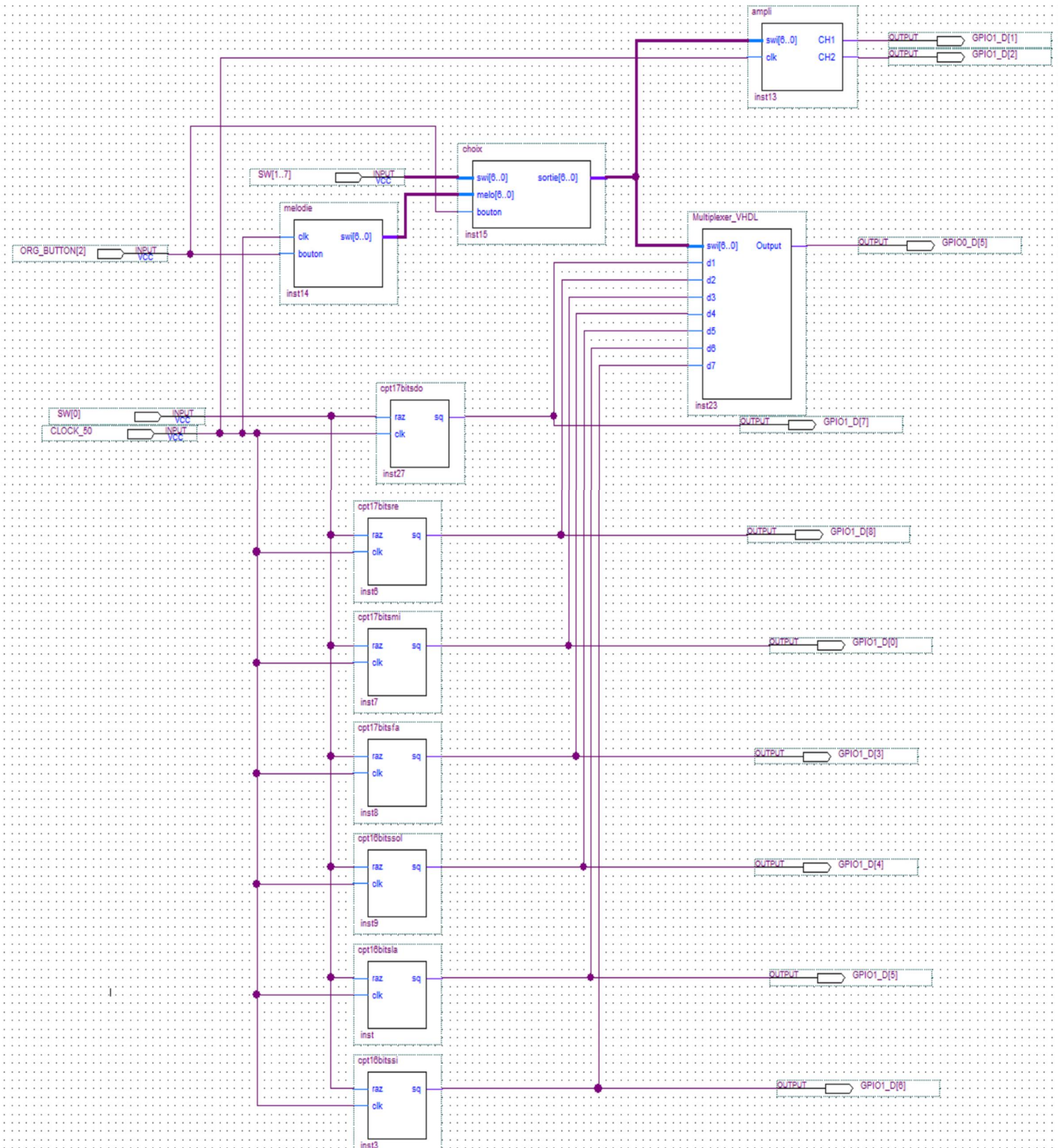


Figure 4 Diagramme en block

Fonctions en VHDL

- Création des fréquences :

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;

entity cpt17bitsre is
  port(
    raz, clk : in std_logic;
    sq : out std_logic
  );
end cpt17bitsre;

architecture Behavioral of cpt17bitsre is
  signal total: STD_LOGIC_VECTOR(16 DOWNTO 0);
begin
  cpt : process(raz,clk)
  begin
    if raz = '1' then -- description asynchrone
      total <= "0000000000000000";
      elsif ( clk 'event and clk='1' ) then-- description synchrone
        total<=total+1;
      end if;
      if(total="10100110010001011")
      then total <= "0000000000000000";

      end if;
    end process;

    sq <= total(16); --hors processus
  end Behavioral;
```

Figure 5 Code pour générer le ré

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;

entity cpt17bitsdo is
  port(
    raz, clk : in std_logic;
    sq : out std_logic
  );
end cpt17bitsdo;

architecture Behavioral of cpt17bitsdo is
  signal total: STD_LOGIC_VECTOR(16 DOWNTO 0);
begin
  cpt : process(raz,clk)
  begin
    if raz = '1' then -- description asynchrone
      total <= "0000000000000000";
      elsif ( clk 'event and clk='1' ) then-- description synchrone
        total<=total+1;
      end if;
      if(total="10111010101000101")|
      then total <= "0000000000000000";

      end if;
    end process;

    sq <= total(16); --hors processus
  end Behavioral;
```

Figure 6 Code pour générer le do


```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;

entity cpt17bitsfa is
  port(
    raz, clk : in std_logic;
    sq : out std_logic
  );
end cpt17bitsfa;

architecture Behavioral of cpt17bitsfa is
  signal total: STD_LOGIC_VECTOR(16 DOWNT0 0);
begin
  cpt : process(raz,clk)
  begin
    if raz = '1' then -- description asynchrone
      total <= "0000000000000000";
      elsif ( clk 'event and clk='1' ) then-- description synchrone

      total<=total+1;
      end if;
      if(total="10001011110100010")
      then total <= "0000000000000000";

      end if;
    end process;

    sq <= total(16); --hors processus
  end Behavioral;

```

Figure 7 Code pour générer le fa

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;

entity cpt17bitsmi is
  port(
    raz, clk : in std_logic;
    sq : out std_logic
  );
end cpt17bitsmi;

architecture Behavioral of cpt17bitsmi is
  signal total: STD_LOGIC_VECTOR(16 DOWNT0 0);
begin
  cpt : process(raz,clk)
  begin
    if raz = '1' then -- description asynchrone
      total <= "0000000000000000";
      elsif ( clk 'event and clk='1' ) then-- description synchrone

      total<=total+1;
      end if;
      if(total="10010100001000011")
      then total <= "0000000000000000";

      end if;
    end process;

    sq <= total(16); --hors processus
  end Behavioral;

```

Figure 8 Code pour générer le mi

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;

entity cpt16bitssol is
  port(
    raz, clk : in std_logic;
    sq : out std_logic
  );
end cpt16bitssol;

architecture Behavioral of cpt16bitssol is
  signal total: STD_LOGIC_VECTOR(15 DOWNTO 0);
begin
  cpt : process(raz,clk)
  begin
    if raz = '1' then -- description asynchrone
      total <= "0000000000000000";
    elsif ( clk 'event and clk='1' ) then-- description synchrone

      total<=total+1;
    end if;
    if(total="1111100100100000")
    then total <= "0000000000000000";

    end if;
  end process;

  sq <= total(15); --hors processus
end Behavioral;

```

Figure 9 Code pour générer le sol

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;

entity cpt16bitsla is
  port(
    raz, clk : in std_logic;
    sq : out std_logic
  );
end cpt16bitsla;

architecture Behavioral of cpt16bitsla is
  signal total: STD_LOGIC_VECTOR(15 DOWNTO 0);
begin
  cpt : process(raz,clk)
  begin
    if raz = '1' then -- description asynchrone
      total <= "0000000000000000";
    elsif ( clk 'event and clk='1' ) then-- description synchrone

      total<=total+1;
    end if;
    if(total="1101110111110010")
    then total <= "0000000000000000";

    end if;
  end process;

  sq <= total(15); --hors processus
end Behavioral;

```

Figure 10 Code pour générer le la


```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;

entity cpt16bitssi is
  port(
    raz, clk : in std_logic;
    sq : out std_logic
  );
end cpt16bitssi;

architecture Behavioral of cpt16bitssi is
  signal total: STD_LOGIC_VECTOR(15 DOWNT0 0);
begin
  cpt : process(raz,clk)
  begin
    if raz = '1' then -- description asynchrone
      total <= "0000000000000000";
    elsif ( clk 'event and clk='1' ) then-- description synchrone

      total<=total+1;
    end if;
    if(total="1100010110111011")
    then total <= "0000000000000000";

    end if;
  end process;

  sq <= total(15); --hors processus
end Behavioral;

```

Figure 11 Code pour générer le si

- Multiplexeur

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Multiplexer_VHDL is
  port
  (
    swi : in std_logic_vector(6 DOWNT0 0);
    d1,d2,d3,d4,d5,d6,d7 : in std_logic;

    Output: out std_logic
  );
end entity Multiplexer_VHDL;

architecture Behavioral of Multiplexer_VHDL is
begin
  process (d1, d2, d3, d4, d5, d6, d7, swi) is
  begin
    case swi is
      when "0000001" => Output <= d1;
      when "0000010" => Output <= d2;
      when "0000100" => Output <= d3;
      when "0001000" => Output <= d4;
      when "0010000" => Output <= d5;
      when "0100000" => Output <= d6;
      when "1000000" => Output <= d7;
      when others => Output <= '0';
    end case;
  end process;
end architecture Behavioral;

```

Figure 12 Code du multiplexeur

- Mélodie

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity melodie is
  port
  (
    clk : in std_logic;
    bouton : in std_logic;

    swi : out std_logic_vector(6 DOWNTO 0)
  );
end entity melodie;

architecture Behavioral of melodie is
  signal cpt: integer range 0 to 870000000;

begin

  process (clk, bouton) is
  begin

    if bouton='0' then

      if clk'event and clk='1' then
        cpt<=cpt+1;

        if(cpt=1) then --do--
          swi<="0000001";

          elsif(cpt=100000000) then --sol--
            swi<="0010000";

            elsif(cpt=210000000) then --la--
              swi<="0100000";

              elsif(cpt=320000000) then --sol--
                swi<="0010000";

                elsif(cpt=430000000) then --fa--

              elsif(cpt=540000000) then --mi--
                swi<="0000100";

                elsif(cpt=650000000) then --ré--
                  swi<="0000010";

                  elsif(cpt=760000000) then --do--
                    swi<="0000001";

                    end if;
                  end if;

                else
                  swi<="0000000";

                end if;
              end process;
            end architecture Behavioral;
```

Figure 13 Code de la mélodie

- Choix de mode de fonctionnement : notes simples/mélodie

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity choix is
  port
  (
    swi : in std_logic_vector(6 DOWNTO 0);
    melo : in std_logic_vector(6 DOWNTO 0);
    bouton : in std_logic;

    sortie : out std_logic_vector(6 DOWNTO 0)
  );
end entity choix;

architecture Behavioral of choix is

  signal cpt: integer range 0 to 110000000;

begin

  process (melo, swi, bouton) is
  begin

    if bouton='0' then
      sortie <= melo;

    else
      sortie <= swi;

    end if;

  end process;
end architecture Behavioral;
```

Figure 14 Code du programme "choix"

- Modification de l'amplitude du signal

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity ampli is
  port
  (
    swi : in std_logic_vector(6 DOWNTO 0);
    clk : in std_logic;

    CH1 : out std_logic;
    CH2 : out std_logic
  );
end entity ampli;

architecture Behavioral of ampli is
  signal cpt: integer range 0 to 110000000;

begin

  process (clk, swi) is
  begin

    if (swi/="0000000") then

      if clk'event and clk='1' then
        cpt<=cpt+1;

        if(cpt=1) and (swi/="0000000") then --montée premier niveau--
          CH1<='1';
          CH2<='0';

          elsif(cpt=5000000) and (swi/="0000000") then --montée deuxième niveau--
          CH1<='0';
          CH2<='1';

          elsif(cpt=10000000) and (swi/="0000000") then --montée au maximum--
          CH1<='0';
          CH2<='0';

          elsif(cpt=80000000) then --redescence deuxième niveau--
          CH1<='0';
          CH2<='1';

          elsif(cpt=85000000) then --redescence premier niveau--
          CH1<='1';
          CH2<='0';

          elsif(cpt=90000000) then --redescence à 0--
          CH1<='1';
          CH2<='1';

          end if;
        end if;

      else
        CH1<='1';
        CH2<='1';

      end if;
    end process;
  end architecture Behavioral;

```

Figure 15 Programme de gestion de l'amplitude